

OBJECTIVE:

Designing a universal shift register using flip-flops and multiplexers.

COMPONENT ANALYSIS:

Name	Quantity
i) Trainers board	— 1 piece
ii) IC extractor	— 1 piece
iii) IC (Dual 4x1 MUX) 74153	— 2 pieces
iv) IC (Dual D-FF) 7474	— 2 pieces
v) Magnifier	— 1 piece
vi) Handbook	— 1 piece
vii) Wires	

PROBLEM SPECIFICATION:

Design and implement a 4-bit universal shift register.


EXCITATION TABLE:

Input					Output				Mode
CLEAR	Clock	S_0	S_1	P_i	A_3	A_2	A_1	A_0	
0	X	X	X	X	0	0	0	0	Asynchronous clear
1	X	0	0	X	A_3	A_2	A_1	A_0	Hold
1	↑	0	1	A_{i+1}	I_R	A_3	A_2	A_1	Shift right
1	↑	1	0	A_{i+1}	A_2	A_1	A_0	I_L	Shift left
1	↑	1	1	A_i	I_3	I_2	I_1	I_0	Parallel load

DESIGN:

Parallel outputs

preset?

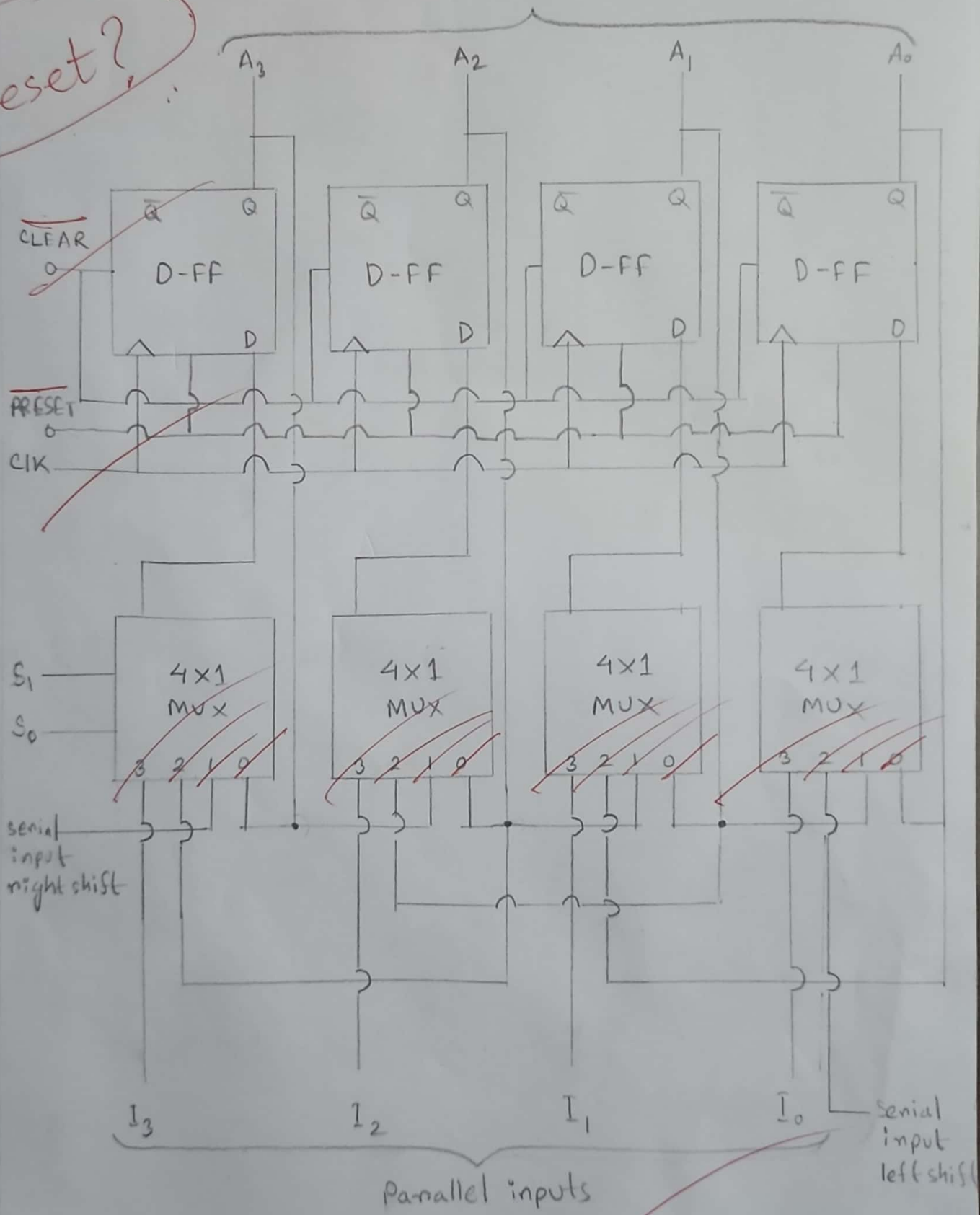

CIRCUIT DIAGRAM:

